

Electricity

1. What does an electric circuit mean?

Solution:

A continuous closed path made of electric components through which an electric current flows is known as an electric circuit. A simple circuit consists of the following components:

(a) Conductors

(b) Cell

(c) Switch

(d) Load

2. Define the unit of current.

Solution:

The unit of current is ampere. Ampere is defined by the flow of one coulomb of charge per second.

3. Calculate the number of electrons constituting one coulomb of charge.

Solution:

The value of the charge of an electron is 1.6×10^{-19} C.

According to charge quantization,

$Q = nq_e$, where n is the number of electrons and q_e is the charge of an electron.

Substituting the values in the above equation, the number of electrons in a coulomb of charge can be calculated as follows:

$$1 \text{ C} = n \times 1.6 \times 10^{-19}$$
$$n = \frac{1}{1.6 \times 10^{-19}} = 6.25 \times 10^{18}$$

Therefore, the number of electrons constituting one coulomb of charge is 6.25×10^{18} .

In text 12.2 Page: 202

4. Name a device that helps to maintain a potential difference between across a conductor.

Solution : Battery

5. What is meant by saying that the potential difference between two points is 1 v?

Solution : The potential difference between two points is said to be 1 volt, if 1 joule of work is to be done for moving charge of 1 coulomb from one point to another.

6. How much energy is given to each coulomb of charge passing through a 6-volt battery?

Solution :

Potential difference (V) = 6 V

Charge (Q) = 1 C

Energy = total work done (W) = $Q \times V = 1 \times 6 = 6$ joule.

7. On what factor does the resistance of a conductor depend?

Solution : The resistance of a conductor depends upon the following factors:

- (a) Length of the conductor
- (b) Cross-sectional area of the conductor
- (c) Material of the conductor
- (d) Temperature of the conductor

8. Will current flow more easily through a thick wire or a thin wire of the same material, when connected to the same source? Why?

Solution : The current flows more easily through a thick wire as compared to thin wire of the same material, when connected to the same source. It is due to the reason that resistance increases with decrease in thickness.

9. Let the resistance of an electric component remains constant while the potential difference across the two ends of the component decreases to half of its former value. What change will occur in the current through it?

Solution : It is given that resistance R of the electrical component remains constant but the potential difference across the ends of the component decreases to half of its value.

Hence, as per Ohm's law, new current also decreases to half of its original value.

10. Why are coils of electric toasters and electric irons made of an alloy rather than a pure metal?

Solution : Coils of electric toasters and electric irons are made of an alloy due to the following reasons:

(i.) Resistivity of an alloy is generally higher than that of pure metal.

(ii.) At high temperature, an alloy does not oxidize readily. Hence, coil of an alloy has longer life.

5. Use the Data in Table To Answer the Following:

Table: Electrical resistivity of some substances at

20°C to 20°C

	Material	Resistivity Ωm
	Silver	1.60×10^{-8}
	Copper	1.62×10^{-8}
	Aluminium	2.63×10^{-8}

Conductor	Tungsten	$5.20 \times 10^{-8} - 5.20 \times 10^{-8}$
	Nickel	$6.84 \times 10^{-8} - 6.84 \times 10^{-8}$
	Iron	$10.0 \times 10^{-8} - 10.0 \times 10^{-8}$
	Chromium	$12.9 \times 10^{-8} - 12.9 \times 10^{-8}$
	Mercury	$94.0 \times 10^{-8} - 94.0 \times 10^{-8}$
	Manganese	$1.84 \times 10^{-8} - 1.84 \times 10^{-8}$
Alloy	Constantan (alloy of Cu and Ni)	$44 \times 10^{-6} - 44 \times 10^{-6}$
	Manganin (alloy of Cu, Mn and Ni)	$49 \times 10^{-6} - 49 \times 10^{-6}$
	Nichrome (alloy of Ni, Cr, Mn and Fe)	$100 \times 10^{-6} - 100 \times 10^{-6}$
Insulator	Glass	$10^{10} \sim 10^{14} - 10^{10} \sim 10^{14}$
	Hard rubber	$10^{13} \sim 10^{16} - 10^{13} \sim 10^{16}$
	Ebonite	$10^{15} \sim 10^{17} - 10^{15} \sim 10^{17}$
	Diamond	$10^{12} \sim 10^{13} - 10^{12} \sim 10^{13}$
	Paper (Dry)	$10^{12} - 10^{12}$

a) Which Among Iron and Mercury is a Better Conductor?

Ans: Resistivity of iron = $10.0 \times 10^{-8} \Omega \text{m}$

Resistivity of mercury = $94.0 \times 10^{-8} \Omega \text{m}$

Resistivity of mercury is more than that of iron. So, iron is a better conductor than mercury because resistivity is inversely proportional to conductivity.


b) Which Material is the Best Conductor?

Ans: Metal with least resistivity is the best conductor. In the above question, according to the table, Silver is the best conductor.

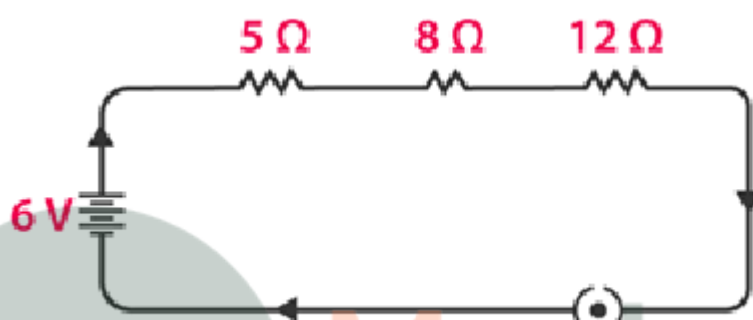1. Draw a schematic diagram of a circuit consisting of a battery of three cells of 2 V each, a 5 Ω resistor, an 8 Ω resistor, and a 12 Ω resistor, and a plug key, all connected in series.

Solution:


A battery of three cells of 2 V each equals to battery of potential 6 V. The circuit diagram below shows three resistors of resistance 12 Ω , 8 Ω and 5 Ω connected in series along with a battery of potential 6 V.



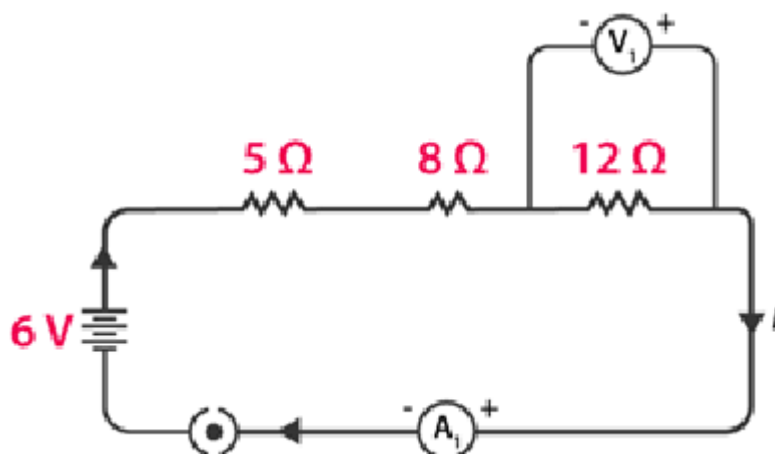2. Redraw the circuit of Question 1, putting in an ammeter to measure the current through the resistors and a voltmeter to measure the potential difference across the 12 Ω resistor. What would be the readings in the ammeter and the voltmeter?

Solution:

An ammeter should always be connected in series with resistors while the voltmeter should be connected in parallel to the resistor to measure the potential difference as shown in the figure below.



Using Ohm's Law, we can obtain the reading of the ammeter and the voltmeter.

The total resistance of the circuit is $5\ \Omega + 8\ \Omega + 12\ \Omega = 25\ \Omega$.

We know that the potential difference of the circuit is 6 V, hence the current flowing through the circuit or the resistors can be calculated as follows:

$$I = V/R = 6/25 = 0.24\text{A}$$

Let the potential difference across the $12\ \Omega$ resistor be V_1 .

From the obtained current V_1 can be calculated as follows:

$$V_1 = 0.24\text{A} \times 12\ \Omega = 2.88\text{ V}$$

Therefore, the ammeter reading will be 0.24 A and the voltmeter reading be 2.88 V.

In text 12.6.2 Page: 216

1. Judge the equivalent resistance when the following are connected in parallel – (a) $1\ \Omega$ and $10^6\ \Omega$, (b) $1\ \Omega$, $10^3\ \Omega$, and $10^6\ \Omega$.

Solution:

(a) When $1\ \Omega$ and 10^6 are connected in parallel, the equivalent resistance is given by

$$\frac{1}{R} = \frac{1}{1} + \frac{1}{10^6}$$

$$R = \frac{10^6}{1 + 10^6} \approx \frac{10^6}{10^6} = 1\ \Omega$$

Therefore, the equivalent resistance is $1\ \Omega$.

(b) When $1\ \Omega$, $10^3\ \Omega$, and $10^6\ \Omega$ are connected in parallel, the equivalent resistance is given by

$$\frac{1}{R} = \frac{1}{1} + \frac{1}{10^3} + \frac{1}{10^6}$$

Solving, we get

$$R = \frac{10^6 + 10^3 + 1}{10^6} = \frac{1000000}{1000001} = 0.999\ \Omega$$

Therefore, the equivalent resistance is $0.999\ \Omega$.

15. An electric lamp of $100\ \Omega$, a toaster of resistance $50\ \Omega$ and a water filter of resistance $500\ \Omega$ are connected in parallel to a 220 V source. What is the

resistance of an electric iron connected to the same source that takes as much current as all three appliances, and what is the current through it?

Solution :

Here, voltage (V) = 220 V

$R_1 = 100\ \Omega$, $R_2 = 50\ \Omega$ and $R_3 = 500\ \Omega$

$$1/R = 1/R_1 + 1/R_2 + 1/R_3 \text{ ---}$$

$$1/R = 1/100 + 1/50 + 1/500 = 16/500$$

$$R = 500/16 = 31.25\ \Omega$$

The resistance of electric iron, which draws as much current as all three appliances take together = $R = 31.25\ \Omega$.

Current passing through electric iron (I) = $V/R = 220/31.25 = 7.04\text{ A}$.

16. What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?


Solution : Advantage of connecting electrical devices in parallel with the battery are as follows:

- (i) Voltage across each connecting electrical device is same and device take current as per its resistance.
- (ii) Separate on/off switches can be applied across each device.
- (iii) Total resistance in parallel circuit decreases, hence, a great current may be drawn from cell.
- (iv) If one electrical device is damaged; then other devices continue to work properly.

17. How can three resistors of resistance 2 Ω , 3 Ω and 6 Ω be connected to give a total resistance of (a) 4 Ω (b) 1 Ω ?

Solution :

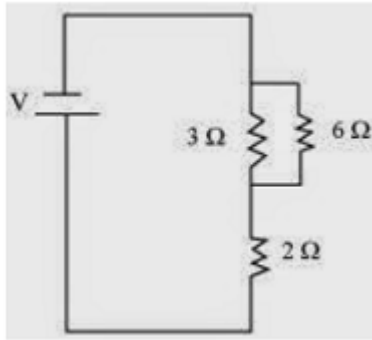(a) If we connect resistance of $3\ \Omega$ and $6\ \Omega$ in parallel and then resistance of $2\ \Omega$ is connected in series of the combination, then total resistance of combination is $4\ \Omega$.



(b) If all the three resistance are joined in parallel the resultant resistance will be $1\ \Omega$.



18. What is (a) the highest, (b) the lowest total resistance that can be secured by combination of four resistances of $4\ \Omega$, $8\ \Omega$, $12\ \Omega$ and $24\ \Omega$?

Solution :

(a) To obtain highest resistance, all the four resistances must be connected in series arrangement. In that case resultant $R = R_1 + R_2 + R_3$

$$= 4 + 8 + 12 = 24\ \Omega$$

(b) To obtain lowest resistance, all the four resistance must be connected in parallel arrangement. $1/R = 1/R_1 + 1/R_2 + 1/R_3$

$$= \frac{1}{4} + \frac{1}{8} + \frac{1}{12} + \frac{1}{24} = \frac{6}{24}\ \Omega$$

$$= \frac{24}{24} = 1\ \Omega$$

1. Why Does the Cord of an Electric Heater Not Glow While the Heating Element Does?

Ans: Heat produced in a system is proportional to its resistance.

The resistance of the heating element is more; so more heat is produced and so it glows.

Also, the resistance of wire is less; so, the heat produced is also less. Hence, the wire does not glow but the heating element does.

2. Compute the Heat Generated While Transferring

96000 C of Charge in One Hour Through a Potential Difference of

50 V

.

Ans: The amount of heat

$H = I^2 R t$

produced is given by the Joule's law of heating as

$$H = V I t \quad H = V I t$$

Where,
Voltage,

$$V = 50 \text{ V} \quad V = 50 \text{ V}$$

Time,

$$t = 1 \text{ h} = 1 \times 60 \times 60 \text{ s} \quad t = 1 \text{ h} = 1 \times 60 \times 60 \text{ s}$$

$$H = V I t \quad H = V I t$$

$$\Rightarrow H = V \cdot q \quad \Rightarrow H = V \cdot q$$

$$\Rightarrow H = V \cdot q \quad \Rightarrow H = V \cdot q$$

$$\Rightarrow H = 50 \times 96000 \quad \Rightarrow H = 50 \times 96000$$

$$\Rightarrow H = 4.8 \times 10^6 \text{ J} \quad \Rightarrow H = 4.8 \times 10^6 \text{ J}$$

Thus, heat produced while transferring the charge is $H = 4.8 \times 10^6 \text{ J}$.

3. An Electric Iron of Resistance

20 Ω

Takes a Current of

5 A

. Calculate the Heat Developed in

30 s

•
Ans: The amount of

$$(H)(H)$$

heat produced is given by the Joule's law of heating as

$$H = VIt = I^2 R t \quad H = VIt = I^2 R t$$

•
Where,

Current,

$$I = 5 \text{ A} \quad I = 5 \text{ A}$$

Time,

$$t = 30 \text{ s} \quad t = 30 \text{ s}$$

Resistance

$$R = 20 \Omega \quad R = 20 \Omega$$

$$H = I^2 R t \quad H = I^2 R t$$

$$\Rightarrow H = 5^2 \times 20 \times 30 \Rightarrow H = 5^2 \times 20 \times 30$$

$$\Rightarrow H = 1.5 \times 10^4 \text{ J} \Rightarrow H = 1.5 \times 10^4 \text{ J}$$

Therefore, the amount of heat developed in the electric iron is $H = 1.5 \times 10^4 \text{ J}$.

Intext Exercise 7

1. What Determines the Rate at Which Energy is Delivered by a Current?

Ans: The rate at which energy is delivered by a current or consumed by the appliance is the power of the appliance.

2. An Electric Motor Takes

$$5 \text{ A} \quad 5 \text{ A}$$

from a

$$220 \text{ V} \quad 220 \text{ V}$$

line. Determine the Power of the Motor and the Energy Consumed in 22 hrs.

Ans: Power

$$(P)(P)$$

is given by the expression

$$P = VI \quad P = VI$$

•

Where,

Voltage,

$$V = 220 \text{ V} \quad V = 220 \text{ V}$$

Current,

$$I = 5 \text{ A} \quad I = 5 \text{ A}$$

$$P = 220 \times 5 = 1100 \text{ W} \quad P = 220 \times 5 = 1100 \text{ W}$$

Energy consumed by the motor = $P \times t = P \times t$

Where,

Time,

$$t = 2 \text{ h} = 2 \times 60 \times 60 = 7200 \text{ s} \quad t = 2 \text{ h} = 2 \times 60 \times 60 = 7200 \text{ s}$$

$$\Rightarrow P = 1100 \times 7200 \Rightarrow P = 1100 \times 7200$$

Therefore, the power of the motor

$$= 1100 \text{ W} \quad = 1100 \text{ W}$$

Energy consumed by the motor = $7.92 \times 10^6 \text{ J} = 7.92 \times 10^6 \text{ J}$.

NCERT Exercise

1. A Piece of Wire of Resistance R is Cut into Five Equal Parts. These parts are then Connected in Parallel. If the Equivalent Resistance of this Combination is

$$R', \text{ then the Ratio}$$

, then the Ratio

$$R/R' \quad R/R'$$

is

a. 125125

b. 1515

c. 55

d. 2525

Ans: Relation between resistance and current is $R \propto l$ or $R \propto l$.

If the wire is cut into five equal parts, the resistance of each part

$$= R/5 = R/5$$

.

All the five parts are connected in parallel. Hence, equivalent resistance

$$\left(\frac{1}{R}\right) \left(\frac{1}{R'}\right)$$

is given as

$$\frac{1}{R'} = \frac{1}{5R + 5R + 5R + 5R + 5R} = \frac{1}{5 + 5 + 5 + 5 + 5R} = \frac{1}{25R}$$

$$\Rightarrow \frac{1}{R'} = \frac{1}{25R} \Rightarrow \frac{R}{R'} = 25$$

Therefore, the ratio

$$\frac{R}{R'}$$

is 25.

2. Which of the following does not represent electrical power in a circuit?

(a) $I^2 R$

(b) IR^2

(c) VI

(d) V^2/R

Solution:

Answer: b) IR^2

Explanation:

Electrical power is given by the expression $P = VI$. (1)

According to Ohm's law,

$$V = IR$$

Substituting the value of V in (1), we get

$$P = (IR) \times I$$

$$P = I^2 R$$

Similarly, from Ohm's law,

$$I = V/R$$

Substituting the value of I in (1), we get

$$P = V \times V/R = V^2/R$$

From this, it is clear that the equation IR^2 does not represent electrical power in a circuit.

3. An electric bulb is rated 220 V and 100 W. When it is operated on 110 V, the power consumed will be ____.

(a) 100 W

(b) 75 W

(c) 50 W

(d) 25 W

Solution:

Answer: 25 W

Explanation:

The energy consumed by the appliance is given by the expression

$$P = VI = V^2/R$$

The resistance of the light bulb can be calculated as follows:

$$R = V^2/P$$

Substituting the values, we get

$$R = (220)^2/100 = 484 \, \Omega$$

Even if the supply voltage is reduced, the resistance remains the same. Hence, the power consumed can be calculated as follows:

$$P = V^2/R$$

Substituting the value, we get

$$P = (110)^2 V/484 \, \Omega = 25 \, W$$

Therefore, the power consumed when the electric bulb operates at 110 V is 25 W.

4. Two conducting wires of the same material and of equal lengths and equal diameters are first connected in series and then parallel in a circuit across the same potential difference. The ratio of heat produced in series and parallel combinations would be ____.

(a) 1:2

(b) 2:1

(c) 1:4

(d) 4:1

Solution:

Let R_s and R_p be the equivalent resistance of the wires when connected in series and parallel respectively.

For the same potential difference V , the ratio of the heat produced in the circuit is given by

$$\frac{H_s}{H_p} = \frac{\frac{v^2}{R_s} t}{\frac{v^2}{R_p} t} = \frac{R_p}{R_s}$$

The equivalent resistance of resistors connected in series R_s is $R + R = 2R$

The equivalent resistance of resistors connected in parallel R_p is $\frac{1}{\frac{1}{R} + \frac{1}{R}} = \frac{R}{2}$

Hence, the ratio of the heat produced in series and parallel combinations would be

$$\frac{H_p}{H_s} = \frac{\frac{R}{2}}{2R} = \frac{1}{4}$$

Hence, the ratio of the heat produced is 1:4.

28. How is a voltmeter connected in the circuit to measure the potential difference between two points?

Solution : A voltmeter is always connected in parallel to resistance across the point between which the potential difference is to be measured.

29. A copper wire has diameter 0.5 mm and resistivity of $1.6 \times 10^{-8} \text{ m}$. what will be the length of this wire to make its resistance 10? How much does the resistance change if the diameter is doubled?

Solution :

Diameter of wire (d) = 0.5 mm, resistivity (ρ) $1.6 \times 10^{-8} \Omega\text{m}$, resistance (R) = 10 Ω .

$$R = \rho L/A$$

$$L = \pi D^2 R / 4\rho$$

$$= 22 \times (5 \times 10^{-4})^2 / 7 \times 4 \times 1.6 \times 10^{-8} = 122.5 \text{ m}$$

If the diameter is doubled for given length of given material resistance is inversely proportional to the cross-section area of wire.

30. The value of current I flowing in a given resistor for the corresponding values of potential difference V across the resistor are given below:

I(amperes)	0.5	1.0	2.0	3.0	4.0
V(volts)	1.6	3.4	6.7	10.2	13.2

Plot a graph between V and I and calculate the resistance of that resistor.

Solution : From the given data the I-V graph is a straight line as shown below:



The slope of the line gives the value of Resistance(R) as,

$$\text{Slope} = 1/R = BC/AC = 2/6.8$$

$$R = 6.8/2 = 3.4 \, \Omega$$

Therefore, the resistance of register is 3.4Ω .

31. When a 12 v battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.

Solution :

$$\text{Voltage of battery} = V = 12 \, \text{V}, \text{ Current (I)} = 2.5 \, \text{mA} = 2.5 \times 10^{-3} \, \text{A}$$

$$\text{Resistance (R)} = V/I = 12\text{V}/ 2.5 \times 10^{-3} \, \text{A} = 4800 \, \Omega.$$

32. A battery of 9 V is connected in series with resistance of 0.2 Ω , 0.3 Ω , 0.4 Ω , 0.5 Ω and 12 Ω respectively. How much current would flow through the 12 resistor?

Solution :

Potential difference (V) = 9 V.

Total resistance (R) = $R_1 + R_2 + R_3 + R_4 + R_5$

= $0.2 + 0.3 + 0.4 + 0.5 + 12 = 13.4 \Omega$

Current in the circuit (I) = $V/R = 9 \text{ V} / 13.4 \Omega = 0.67 \text{ A}$.

In series circuit same current flows through all the resistance, hence current of 0.67 A will flow through 12 Ω resistor.

10. How Many

resistors (in parallel) are Required to carry

on a

176 Ω 176 Ω

5 A 5 A

220 V 220 V

Line?

Ans: Let's assume the number of resistances to be xx.

The equivalent resistance of resistors connected in parallel is given by

$$\frac{1}{R} = \frac{x}{176} \Rightarrow R = \frac{176}{x}$$

$$\Rightarrow R = 176x \Rightarrow R = 176x$$

Now, Ohm's law is given as

$$V = IR \Rightarrow V = IR$$

$$\Rightarrow R = \frac{V}{I} \Rightarrow R = \frac{V}{I}$$

Where,

Supply voltage,

$$V = 220 \text{ V} \quad V = 220 \text{ V}$$

Current,

$$I = 5 \text{ A} \quad I = 5 \text{ A}$$

So, the equation can be written as,

$$176x = 2205 \quad 176x = 2205$$

$$\Rightarrow x = 17644 \Rightarrow x = 17644$$

$$\Rightarrow x = 4 \Rightarrow x = 4$$

Therefore, four resistors of

$$176 \, \Omega \quad 176 \, \Omega$$

are required to draw the given amount of current.

11. Show How You Would Connect Three Resistors, Each of Resistance


$$6 \, \Omega \quad 6 \, \Omega$$

, so that the combination has a resistance of

a).

$$9 \, \Omega \quad 9 \, \Omega$$

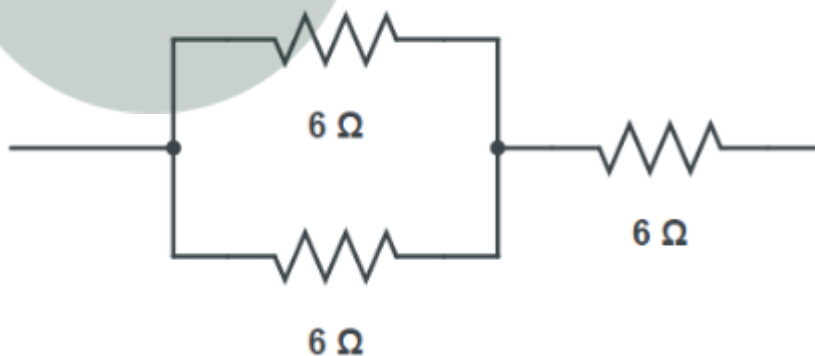Two Resistors in Parallel: Consider the following figure.



Two

$$6 \, \Omega \quad 6 \, \Omega$$

resistors are connected in parallel. Their equivalent resistance will be

$$R = \frac{1}{\frac{1}{6} + \frac{1}{6}} = 3 \, \Omega \quad R = \frac{1}{\frac{1}{6} + \frac{1}{6}} = 3 \, \Omega$$

The third

$$6\ \Omega\ 6\ \Omega$$

resistor is connected in series with

$$3\ \Omega\ 3\ \Omega$$


Hence, the equivalent resistance of the circuit is

$$6\ \Omega + 3\ \Omega = 9\ \Omega .\ 6\ \Omega + 3\ \Omega = 9\ \Omega .$$

b).

$$4\ \Omega\ 4\ \Omega$$

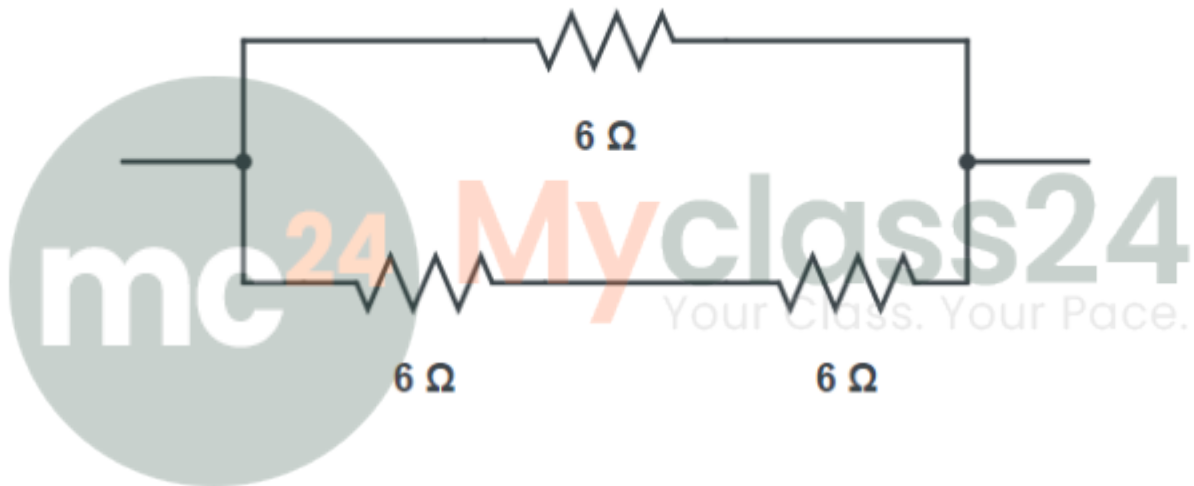Two Resistors in Series: Consider the following figure.



Two

$$6\ \Omega\ 6\ \Omega$$

resistors are connected in series.

Their equivalent resistance will be the sum

$$R=6+6=12\ \Omega\ R=6+6=12\ \Omega$$

The third

$$6\ \Omega\ 6\ \Omega$$

resistor is in parallel with

$$12\ \Omega\ 12\ \Omega$$

Hence, equivalent resistance will be

$$\frac{1}{R_{eq}} = \frac{1}{\frac{1}{12} + \frac{1}{6}} = \frac{12 \times 6}{12+6} = 4 \Omega$$

Therefore, the total resistance is

$$4 \Omega + 4 \Omega$$

12. Several Electric Bulbs Designed to be Used on a 220 V

Electric Supply Line, are Rated

$$10W$$

. How Many Lamps can be Connected in Parallel with Each Other Across the Two Wires of

$$220 V$$

line if the maximum allowable current is

$$5 A$$

?

Ans: Resistance

$$R$$

of one bulb is given by the expression,

$$P = \frac{V^2}{R}$$

$$\Rightarrow R = \frac{V^2}{P}$$

Where,

Supply voltage,

$$V = 220 V$$

Maximum allowable current,

$$I = 5 A$$

Rating of an electric bulb,

$$P = 10 W$$

Resistance of one bulb is $R_1 = \frac{(220)^2}{10} = 4840 \Omega$
 Apply Ohm's law to circuit with all the bulbs,

$$V = IR \quad V = IR$$

R is the total resistance of the circuit for x number of electric bulbs.

$$\Rightarrow R = \frac{V}{I} = \frac{220}{5} = 44 \Omega \Rightarrow R = \frac{V}{I} = \frac{220}{5} = 44 \Omega$$

Resistance of each electric bulb,

$$R_1 = 4840 \Omega \quad R_1 = 4840 \Omega$$

Clearly, since the resistors are connected in parallel,

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_1} + \dots + \frac{1}{R_1} \quad \frac{1}{R} = \frac{1}{R_1} \times x$$

$$\Rightarrow x = \frac{R}{R_1} = \frac{44}{4840} = \frac{1}{110} \Rightarrow x = \frac{R}{R_1} = \frac{44}{4840} = \frac{1}{110}$$

Therefore, 110 electric bulbs can be connected in parallel.

13. A Hot Plate of an Electric Oven Connected to a 220 V

Line has Two Resistance Coils AA and BB , Each of
24 Ω

Resistances, Which May be Used Separately, in Series, or in Parallel. What are the Currents in the Three Cases?

Ans: The given data in the question is as follows:

Supply voltage,

$$V = 220 \text{ V} \quad V = 220 \text{ V}$$

Resistance of one coil,

$$R = 24 \Omega \quad R = 24 \Omega$$

a) Coils are Used Separately:

According to Ohm's law,

$$V = I_1 R_1 \quad V = I_1 R_1$$

Where,

$$I_1$$

is the current flowing through the coil.

$$\Rightarrow I_1 = V/R_1 = 220/24 = 9.166\text{A} \Rightarrow I_1 = V/R_1 = 220/24 = 9.166\text{A}$$

Therefore,

$$9.16\text{ A } 9.16\text{ A}$$

current will flow through each coil when used separately.

b) Coils are Connected in Series:

Total resistance,

$$R_2 = 24\ \Omega + 24\ \Omega = 48\ \Omega \quad R_2 = 24\ \Omega + 24\ \Omega = 48\ \Omega$$

According to Ohm's law,

$$V = I_2 R_2 \quad V = I_2 R_2$$

Where,

I_2 is the current flowing through the series circuit.

$$\Rightarrow I_2 = V/R_2 = 220/48 = 4.58\text{A} \Rightarrow I_2 = V/R_2 = 220/48 = 4.58\text{A}$$

Therefore,

$$4.58\text{ A } 4.58\text{ A}$$

current will flow through the circuit when the coils are connected in series.

c) Coils are Connected in Parallel:

Total resistance, R_3 is given as

$$R_3 = 1/24 + 1/24 = 2/24 = 1/12\ \Omega \quad R_3 = 1/24 + 1/24 = 2/24 = 1/12\ \Omega$$

According to Ohm's law,

$$V = I_3 R_3 \quad V = I_3 R_3$$

Where,

I_3 is the current flowing through the circuit.

$$\Rightarrow I_3 = V/R_3 = 220/12 = 18.33\text{A} \Rightarrow I_3 = V/R_3 = 220/12 = 18.33\text{A}$$

Therefore,

$$18.33\text{ A } 18.33\text{ A}$$

current will flow through the circuit when coils are connected in parallel.

14. Compare the Power Used in the

$$2\ \Omega \quad 2\ \Omega$$

Resistor in Each of the Following Circuits:

a).

$$6\text{ V } 6\text{ V}$$

battery in series with

$$1\ \Omega \quad 1\ \Omega$$

and

$$2\ \Omega\ 2\ \Omega$$

resistors, and

Ans: In the question it is given that

$$V = 6\text{ V}\quad V = 6\text{ V}$$

.

$$1\ \Omega\ 1\ \Omega$$

and

$$2\ \Omega\ 2\ \Omega$$

resistors are connected in series.

Therefore, equivalent resistance of the circuit,

$$R = 1 + 2 = 3\ \Omega\quad R = 1 + 2 = 3\ \Omega$$

According to Ohm's law,

$$V = IR\quad V = IR$$

Where,

I is the current through the circuit

$$\Rightarrow I = \frac{6}{3} = 2\text{ A}\quad \Rightarrow I = \frac{6}{3} = 2\text{ A}$$

In series the same current flows in the entire circuit.

Hence, current flowing through the

$$2\ \Omega\ 2\ \Omega$$

resistor is

$$2\text{ A}\ 2\text{ A}$$

.

Power is given by the expression,

$$P = I^2 R = 2^2 \times 2 = 8\text{ W}\quad P = I^2 R = 2^2 \times 2 = 8\text{ W}$$

b).

$$4\text{ V}\ 4\text{ V}$$

battery in parallel with

$$12\ \Omega\ 12\ \Omega$$

and

$$2\ \Omega\ 2\ \Omega$$

resistors.

Ans: Potential difference,

$$V = 4\ \text{V}\quad V = 4\ \text{V}$$

12 Ω 12 Ω and

$$2\ \Omega\ 2\ \Omega$$

resistors are connected in parallel.

The voltage across each component of a parallel circuit remains the same.

Hence, the voltage across

$$2\ \Omega\ 2\ \Omega$$

resistor will be

$$4\ \text{V}\ 4\ \text{V}$$

Power consumed by

resistor is given by

$$P = \frac{V^2}{R} = \frac{4^2}{2} = 8\ \text{W} \quad P = \frac{V^2}{R} = \frac{4^2}{2} = 8\ \text{W}$$

Therefore, the power used by

$$2\ \Omega\ 2\ \Omega$$

resistor is 8W8W.

38. Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220 V?

Solution :

Current drawn by 1st lamp rated 100 W at 220 V = $P/V = 100/220 = 5/11\ \text{A}$.

Current drawn by 2nd lamp rated 60 W at 220 V = $60/220 = 3/11\ \text{A}$.

In parallel arrangement the total current = $I_1 + I_2 = 3/11 + 5/11 = 8/11 = 0.73\ \text{A}$.

39. Which uses more energy, a 250 W TV set in 1 hour, or a 1200 W toaster in 10 minutes?

Solution :

Energy used by a TV set of power 250 W in 1 hour = $P \times t = 250 \text{ Wh}$.

Energy used by toaster of power 1200 W in 10 minute (10/60 h)

= $P \times t = 1200 \text{ W} \times 10/60 \text{ h} = 200 \text{ Wh}$.

40. An electric heater of resistance 8 Ω draws 15 A from the service mains for 2 hours. Calculate the rate at which heat is developed in the heater.

Solution :

Resistance of electric heater (R) = 8 Ω , current (I) = 15 A.

Rate at which heat developed in the heater = $I^2 R t / t = 15 \times 15 \times 8 = 1800 \text{ W}$.

18. Explain the following.

- Why is the tungsten used almost exclusively for filament of electric lamps?**
- Why are the conductors of electric heating devices, such as bread-toasters and electric irons, made of an alloy rather than a pure metal?**
- Why is the series arrangement not used for domestic circuits?**
- How does the resistance of a wire vary with its area of cross-section?**
- Why copper and aluminium wires are usually employed for electricity transmission?**

Solution:

- The resistivity and melting point of tungsten is very high. Due to this property, it doesn't burn readily when heated. Electric lamps operate at high temperature. Hence, tungsten is a choice of metal for the filament of electric lamps.
- The conductors of electric heating devices are alloys because of their high resistivity. Due to its high resistivity it produces large amount of heat.

c. The voltage is divided in series circuit as result each component in the circuit receives a small voltage because of which the amount of current decreases and the device gets hot and does not work properly. This is the reason why series circuits are not used in domestic circuits.

d. Resistance is inversely proportional to the area of cross section. When the area of cross section increases the resistance decreases and vice versa.

e. Copper and aluminium are good conductors of electricity and have low resistivity because of which they are usually employed for electricity transmission.

